

## 利用 OPA 实现 Bass Boost 案例分享

张方文 *Fabian Zhang*

East China OEM Application Team

### 摘 要

在模拟音箱和耳机驱动系统开发过程中，工程师经常希望利用驱动电路来改善低频/高频响应曲线。在数字系统中，往往通过 EQ 来进行调整，只需要很低的成本就可以满足各种应用。而全模拟系统中要实现 EQ 功能，则需付出更多成本和努力。本文介绍一种利用 Shelving Filter 来实现 Bass Boost 的方法，相对比较简单、成本低廉。

### 目 录

1	Bass Boost 电路的应用场景-----	2
2	Bass Boost 电路理论基础及优化设计-----	3
3	小结-----	7
4	参考资料-----	7

### 图 表

1	1.1 实际喇叭频率响应曲线-----	2
2	2.1a Inverting Shelving Filter 结构图-----	3
3	2.1b. Shelving Filter 频率响应曲线-----	3
4	2.2 目标频率响应曲线-----	4
5	2.3 电路设计-----	5
6	2.4 电路仿真图-----	5
7	2.5 在客户应用电路板上实际量测曲线-----	6

## 1. Bass Boost 调整电路的应用场景

音箱设备对于音乐不同频率成分的还原能力不相同，通常利用频响曲线标识这一特性。抛开是否好听等主观因素，理想的系统频响曲线为一条直线。但是实际应用中，由于结构设计及成本的考量，理想频响曲线是无法实现的。每一个音频设备都有其频率响应曲线。图 1.1 常见动圈式 SPK 频响曲线：

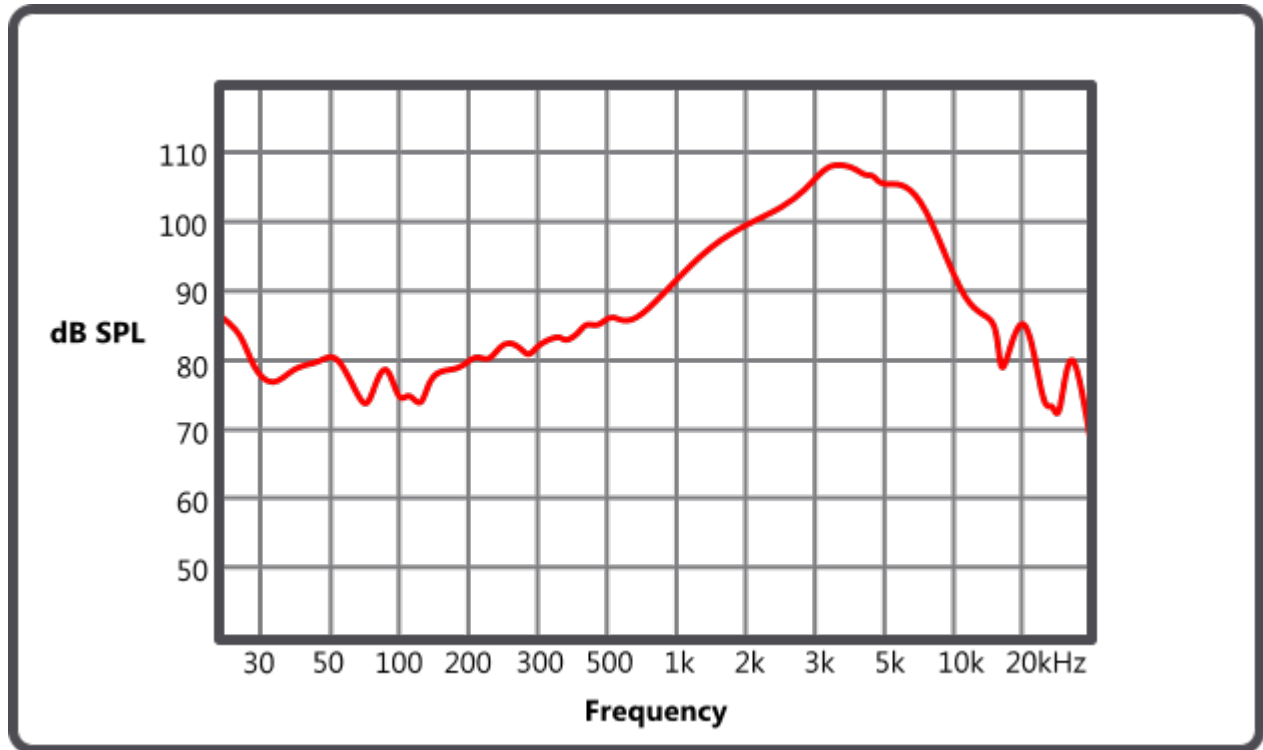


图 1.1 实际喇叭频率响应曲线

从图上可以看出，在 100~1KHz & 10K~20K 喇叭本身电声转换效率较差，为了让系统的频响曲线更接近理想的一条直线，工程师在设计驱动模块时，通常会设计一些电路来调整低频和高频部分的增益，使系统的频率响应曲线更理想化。

## 2. Bass/Treble 调整电路理论基础及优化设计

有源低通 invert Shelving Filter 电路结构及频率特性曲线如图 2.1 所示

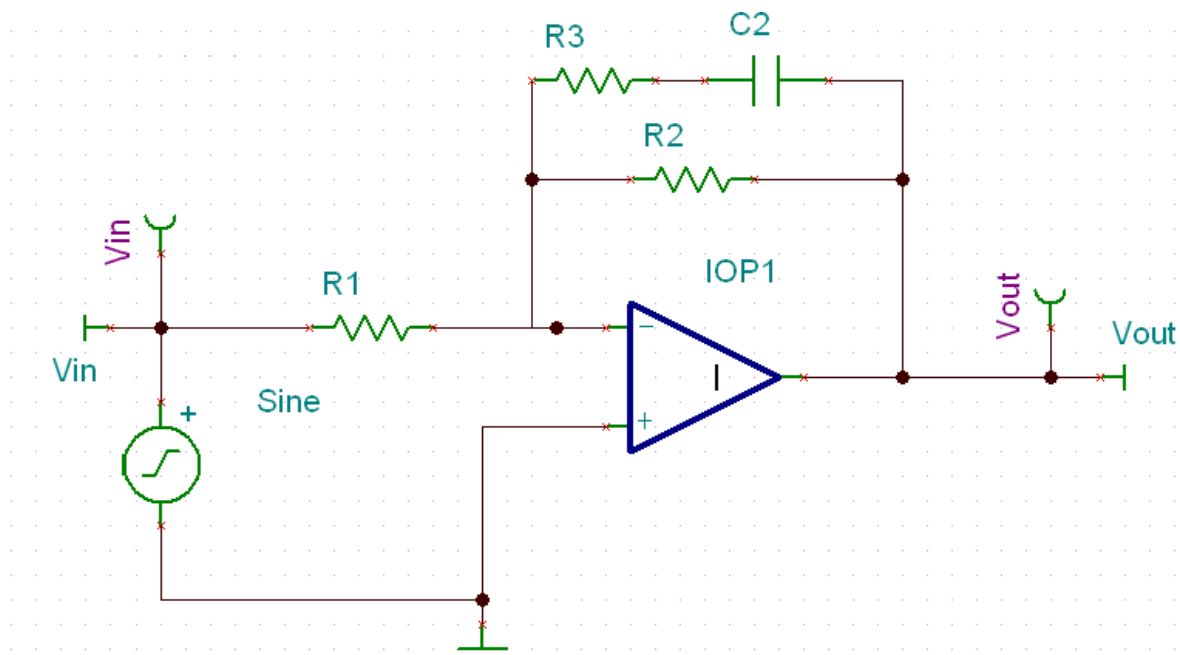


图 2.1a. 有源低通 Inverting Shelving Filter 结构图

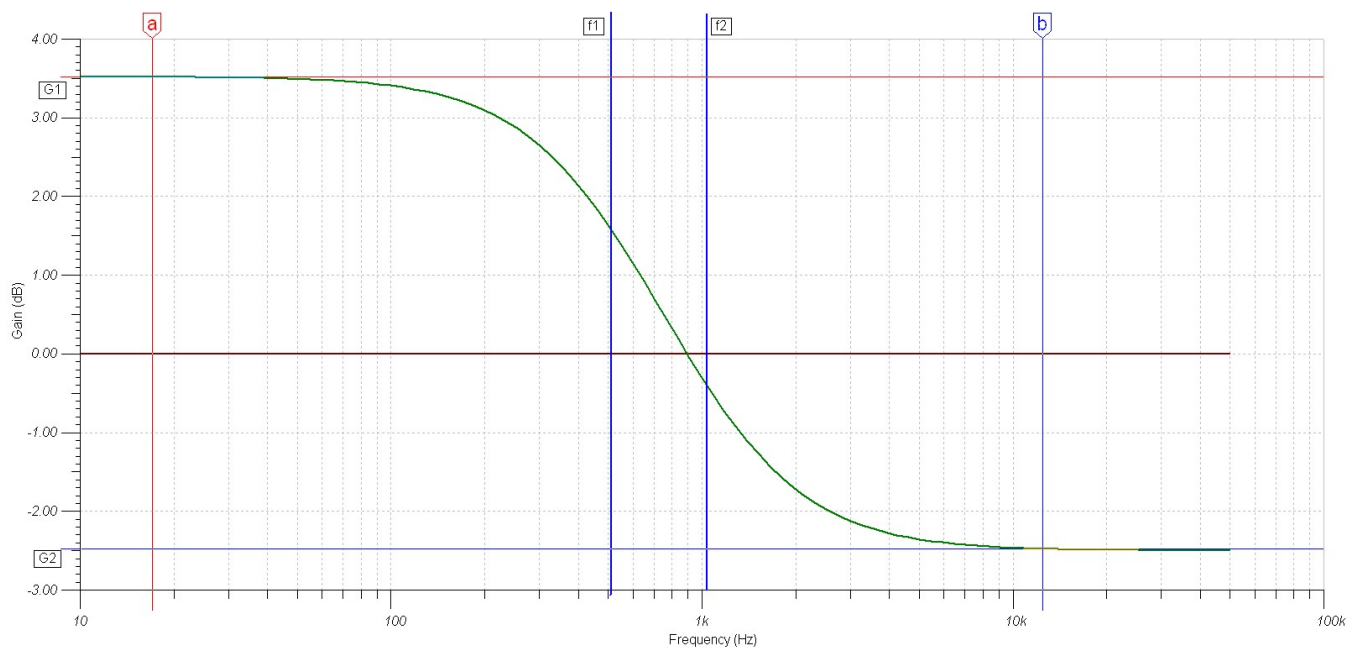


图 2.1b. 有源低通 Inverting Shelving Filter 频率响应曲线

如图 2.1a 所示电路结构，等效反馈阻抗  $R_{fb}$  计算公式如公式 1 所示：

$$R_{fb} = R_2 // R_1(R_3 + 1/SC_2) \quad (1)$$

与当输入信号频率比较低时,  $C_2$  容抗很大, 等效为开路. 此时  $R_{fb}$  约等于  $R_2$ , 由此可得此时通路的增益  $G_1$  为

$$G_1 = R_2/R_1 \quad (2)$$

当输入信号频率较大时,  $C_2$  容抗很小, 等效为闭路, 此时  $R_{fb}$  等效为  $R_2$  与  $R_3$  并联阻抗, 通路通路增益  $G_2$  为:

$$G_2 = (R_2//R_3)/R_1 = (R_2 * R_3)/(R_1 * (R_2 + R_3)) \quad (3)$$

为了更便于分析 Shelving Filter 性能, 同时引入两个频率参数:

$$f_1 = 1/2\pi C_2 (R_2 + R_3) \quad (4)$$

$$f_2 = 1/2\pi C_2 R_3 \quad (5)$$

下面我们根据客户一个应用实例来分析如何选择 Shelving Filter 电容和电阻值. 以满足客户需求. 图 2.2 是客户目标频率响应曲线:

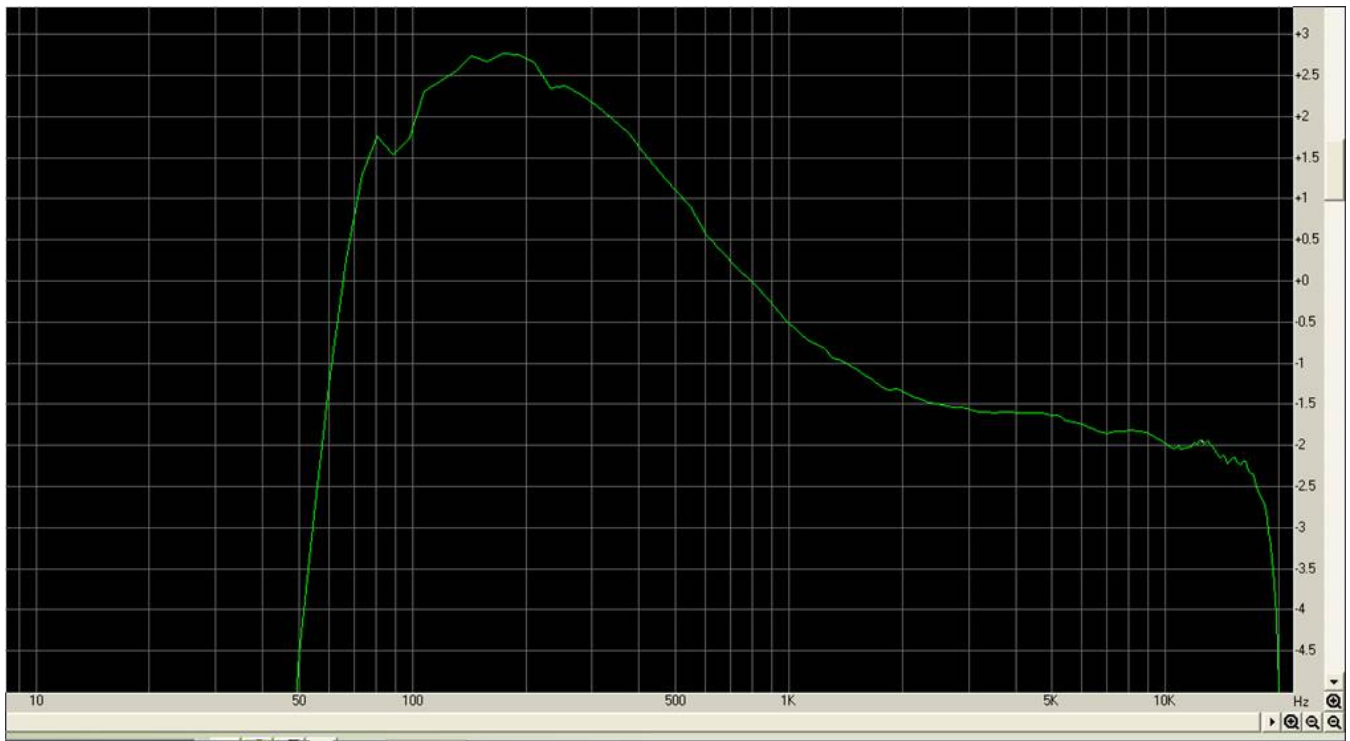


图 2.2 客户目标频率响应曲线

从如图 2.1 所示曲线与 Shelving 低通滤波器频率响应曲线高度一致。因此, 可以设计一个 Shelving Filter 来实现该 Bass Boost 功能. 由图可以直接确定, Shelving Filter 的基本参数  $G_1 = 3\text{dB}$ ,  $G_2 = -1.5\text{dB}$ , 本文中, 为了简化设计与计算, 将目标曲线整体上抬  $1.5\text{dB}$ , 取  $G_2 = 0\text{dB}$ ,  $G_1 = 4.5\text{dB}$ ,  $f_1 = 400\text{Hz}$ ,  $f_2 = 800\text{Hz}$ , 取  $R_2 = R_3$ . 同时设计一个前置高通滤波器达到目前曲线低频抑制效果, 本文利用一个简单的 DC-Blocking 电路来实现.:

根据给定的目标参数，基于 TI DRV632 设计出的电路机构如下：

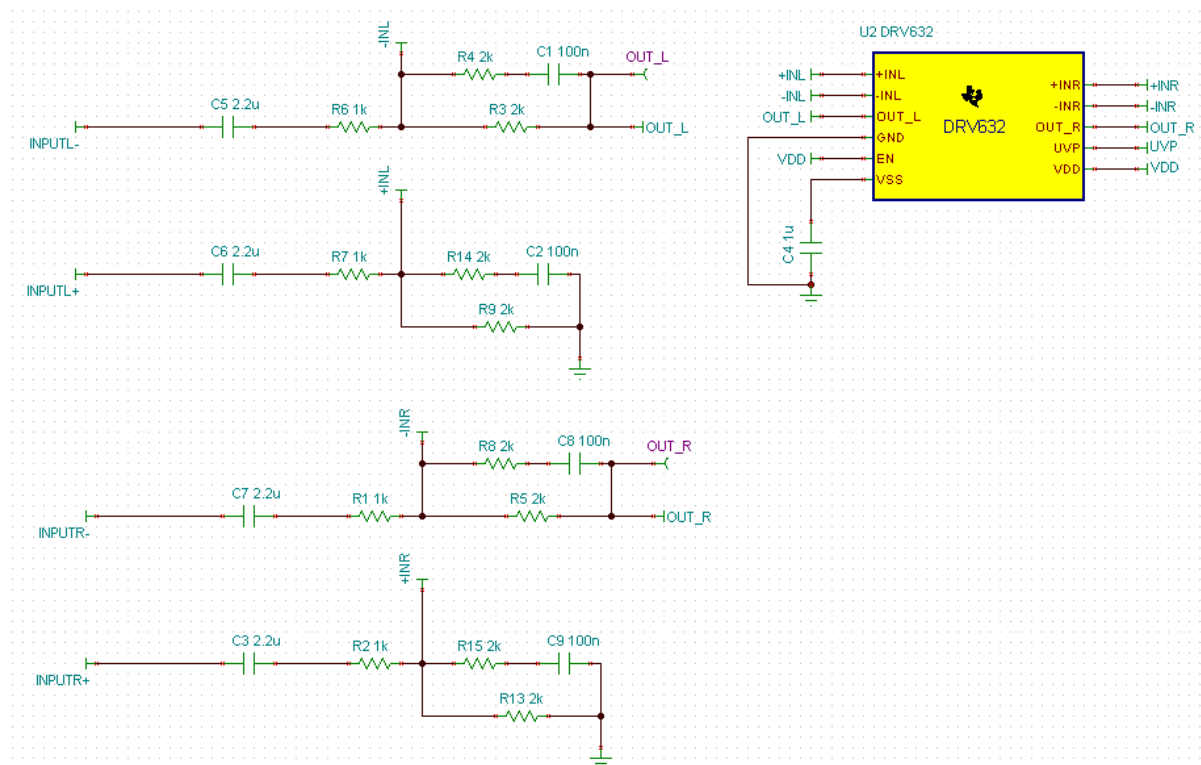


图 2.3 电路设计

AC 仿真图如下：

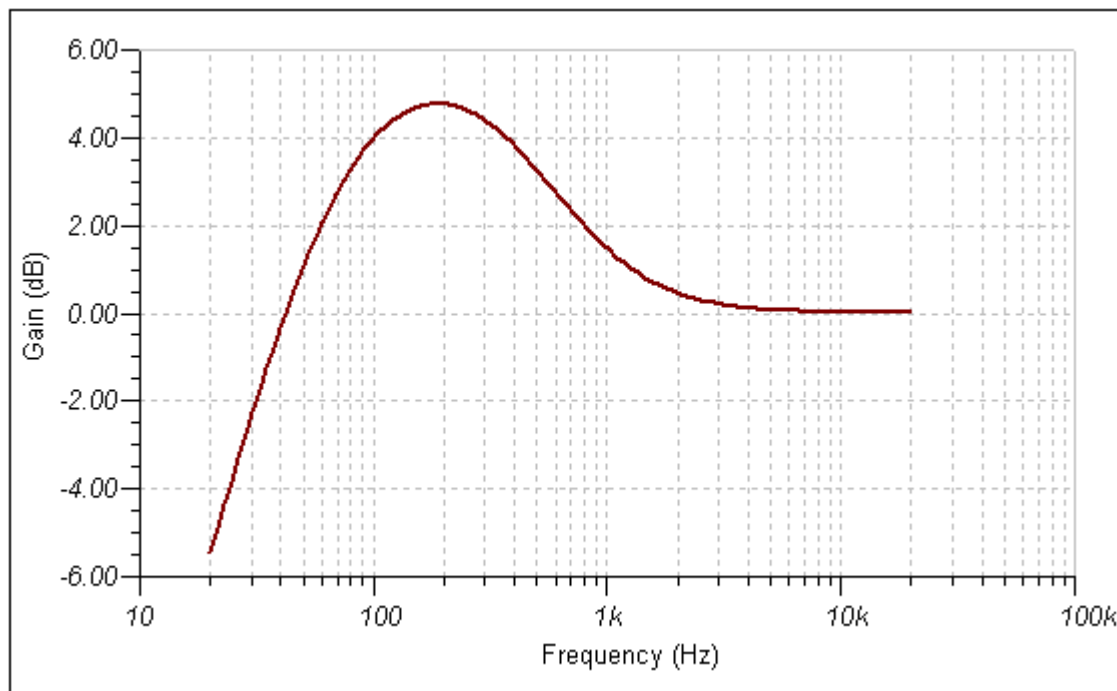


图 2.4 电路仿真图

在客户应用电路上实际量测图 2.5:

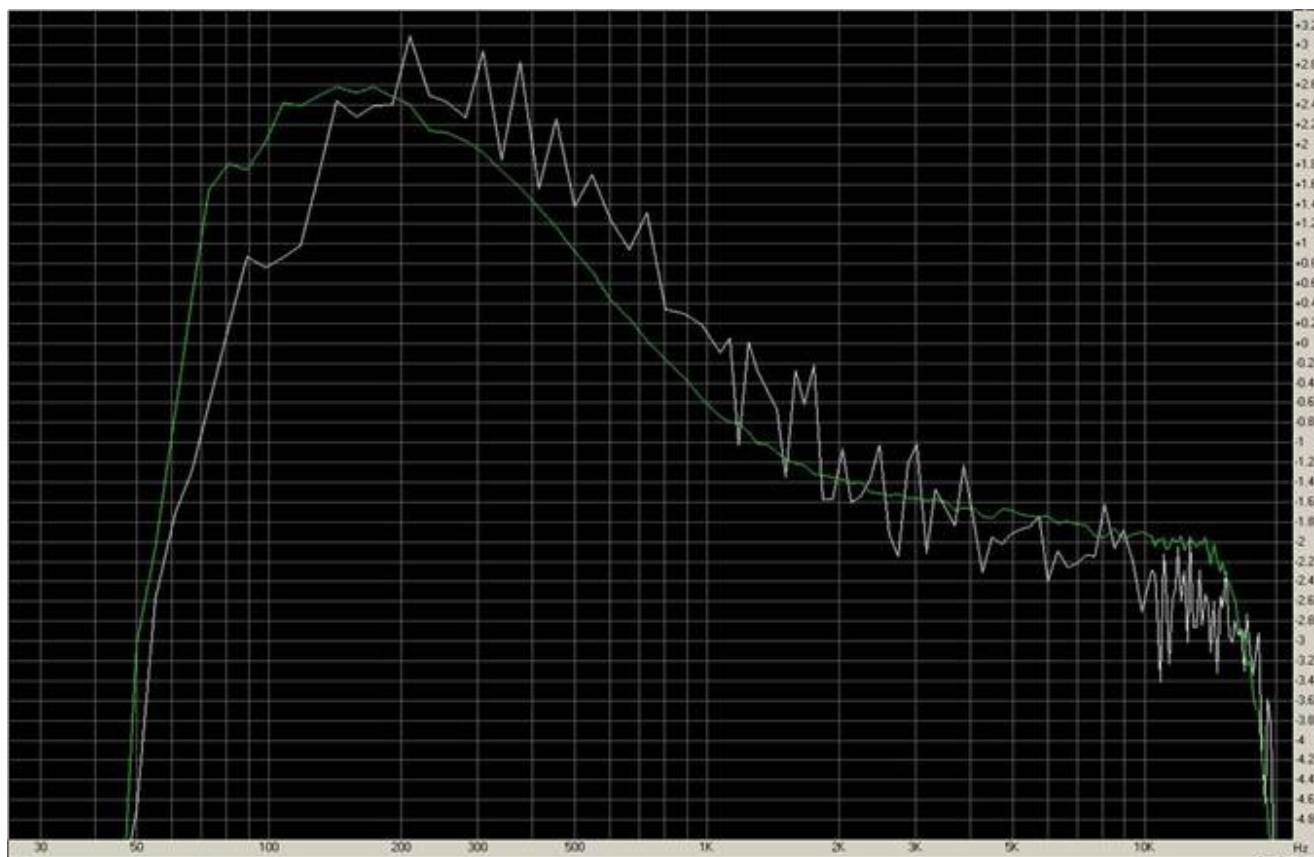


图 2.5 在客户应用电路板上实际量测曲线（白色为实测图）

通过实测图对比可以看出，使用 Shelving Filter 完全可以满足一般客户对于简单 Bass Boost 电路设计需求。

### 3. 小结

本文通过客户实例分析，详细介绍如何利用 Shelving Filter 来实现简单的 Bass Boost。其最主要的特点在于调整目标频率增益的同时，可以让带外的信号不做太大衰减或放大。基于 Shelving Filter 特点，可以更进一步设计出 Treble Boost 电路，甚至可以通过级联，实现任意频段增益控制。对于在无法实现数字 EQ 的系统中，该设计可以帮工程师以更简单快捷成本低廉的方式实现更好品质音乐系统。

### 4. 参考资料

1. DRV632 数据手册----- <http://www.ti.com/lit/ds/symlink/drv632.pdf>;
2. Active Filters-Shelving Filter----- <http://www.linkwitzlab.com/filters.htm#6>

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)